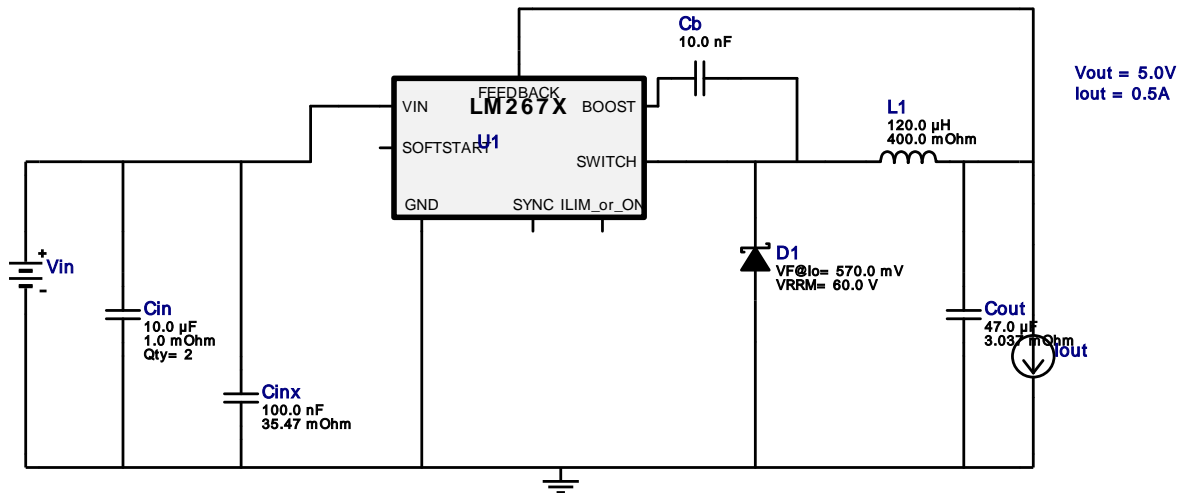







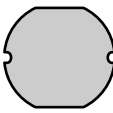
## WEBENCH® Design Report


Design : 1 LM2678SX-5.0/NOPB  
LM2678SX-5.0/NOPB 20V-40V to 5.00V @ 2.5A















1. The small series "trace inductance", particularly from the Switch Output pin, can create a high frequency (10's of MHz) ringing signal at the switch output. If problematic, this ringing can be reduced or eliminated by the use of a series RC damper or snubber network from the switch output to ground. Values of 0.01 uF and 10 ohm are good starting values that may need to be varied depending on the magnitude of parasitic factors in a given design. In an actual end application, these components are normally not required if proper care to minimize trace lengths is taken in the PCB design.







## Electrical BOM


Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cb	TDK	C2012C0G1H103K060AA Series= C0G/NP0	Cap= 10.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.07	 0805 7 mm <sup>2</sup>
Cin	MuRata	GRM32ER71J106KA12L Series= X7R	Cap= 10.0 uF ESR= 1.0 mOhm VDC= 63.0 V IRMS= 6.0 A	2	\$0.30	 1210_280 15 mm <sup>2</sup>
Cinx	Kemet	C0805C104M5RACTU Series= X7R	Cap= 100.0 nF ESR= 35.47 mOhm VDC= 50.0 V IRMS= 1.64 A	1	\$0.01	 0805 7 mm <sup>2</sup>
Cout	MuRata	GRM32ER61C476KE15L Series= X5R	Cap= 47.0 uF ESR= 3.037 mOhm VDC= 16.0 V IRMS= 4.59346 A	1	\$0.17	 1210_280 15 mm <sup>2</sup>
D1	Nexperia	PMEG6010CEH,115	VF@Io= 570.0 mV VRRM= 60.0 V	1	\$0.04	 SOD-123F 12 mm <sup>2</sup>
L1	NIC Components	NPI105C121MTRF	L= 120.0 µH 400.0 mOhm	1	\$0.23	 IND_NPI105C 141 mm <sup>2</sup>

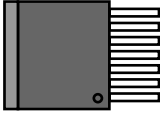Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
U1	Texas Instruments	LM2678SX-5.0/NOPB	Switcher	1	\$2.97	 TS7B 199 mm <sup>2</sup>

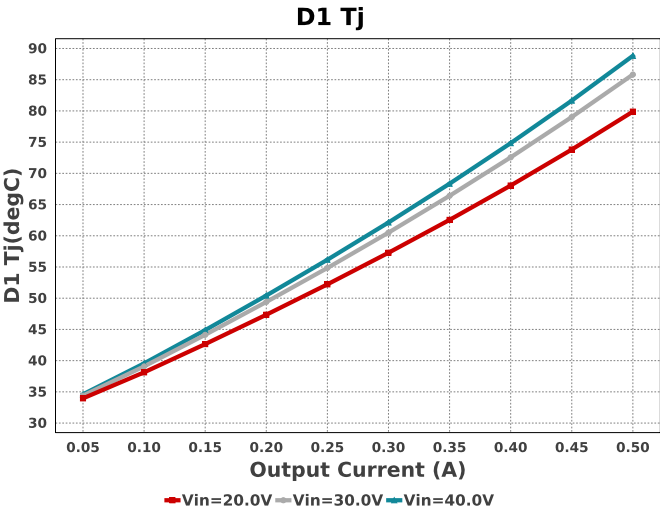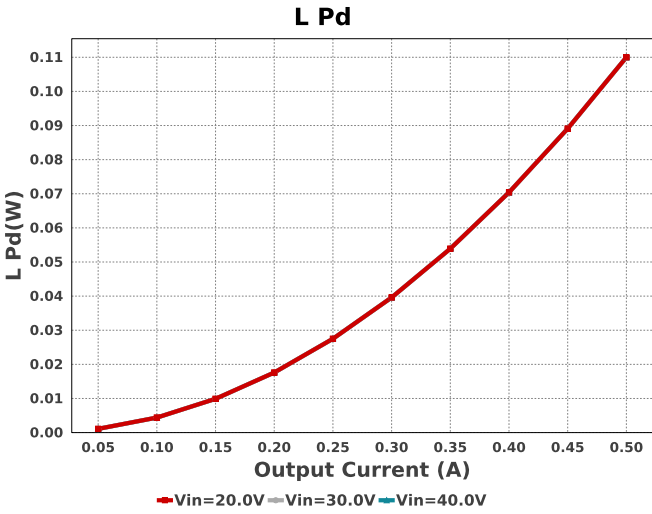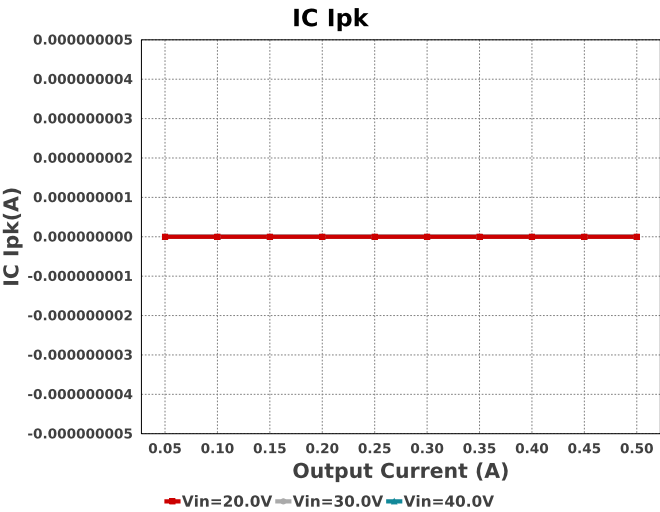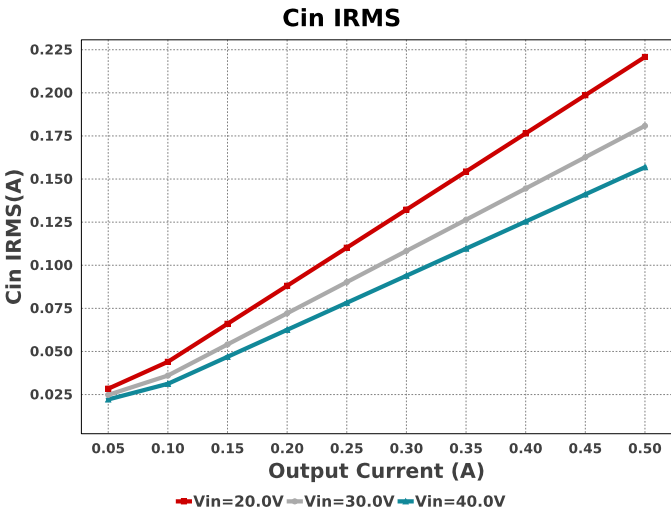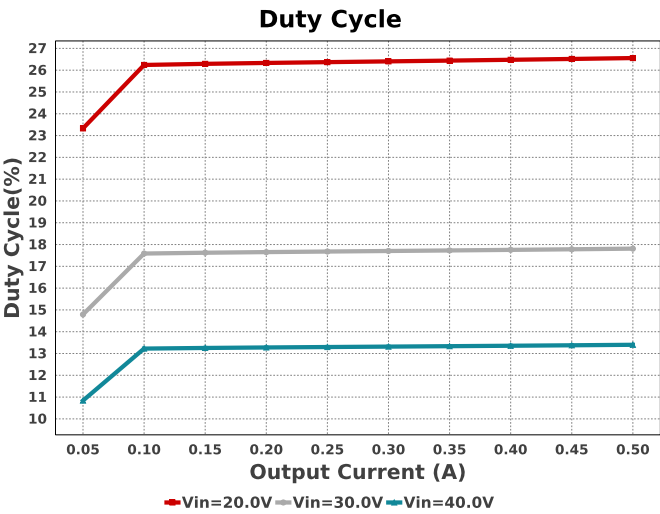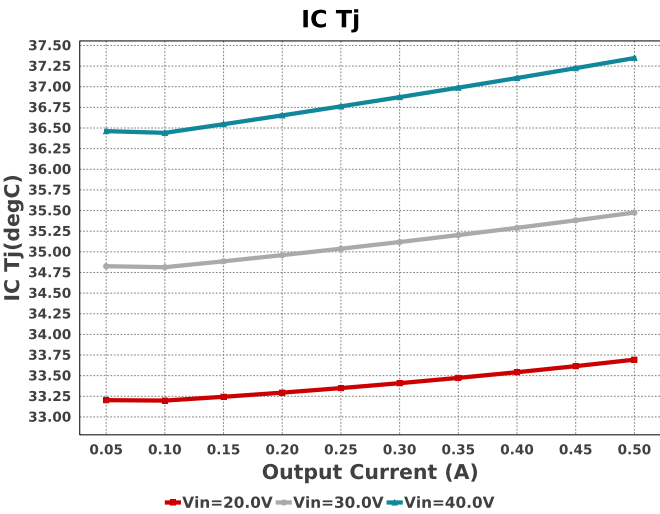

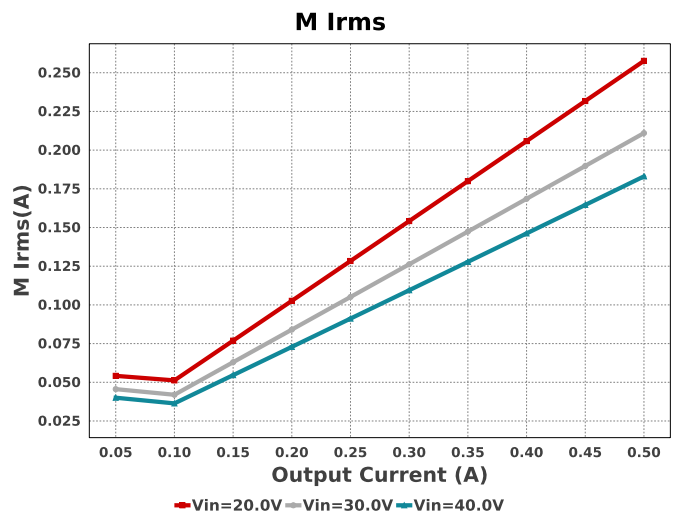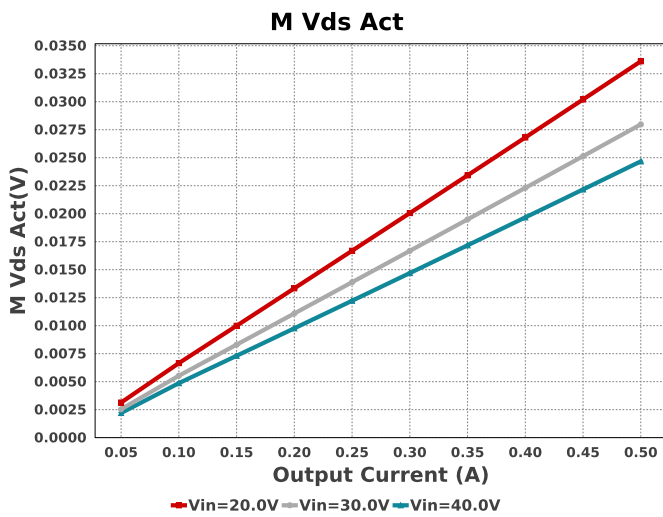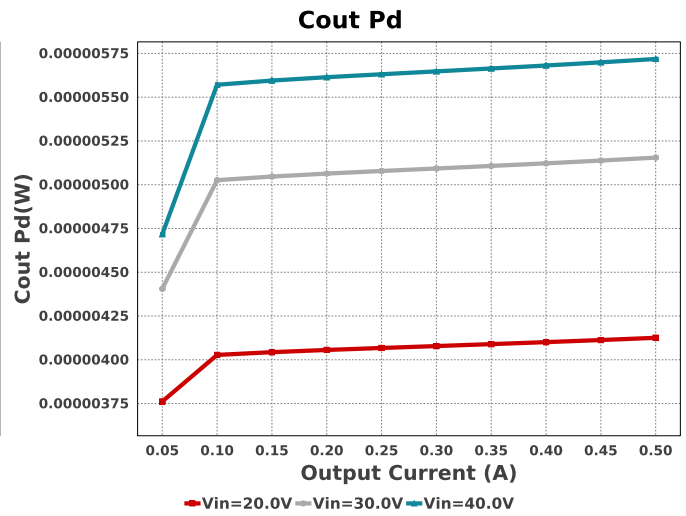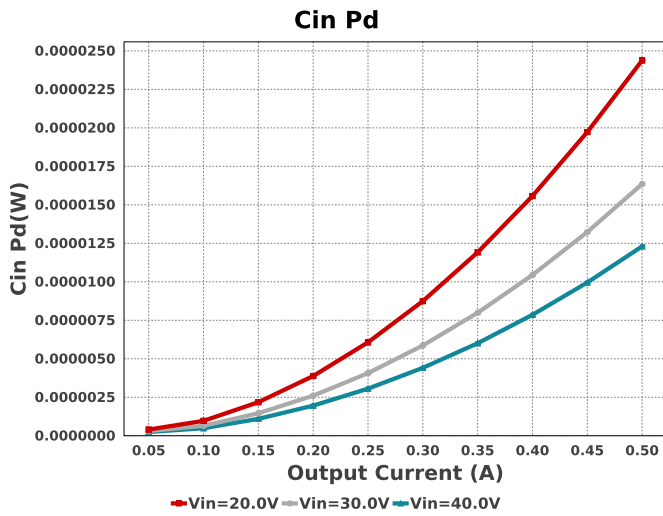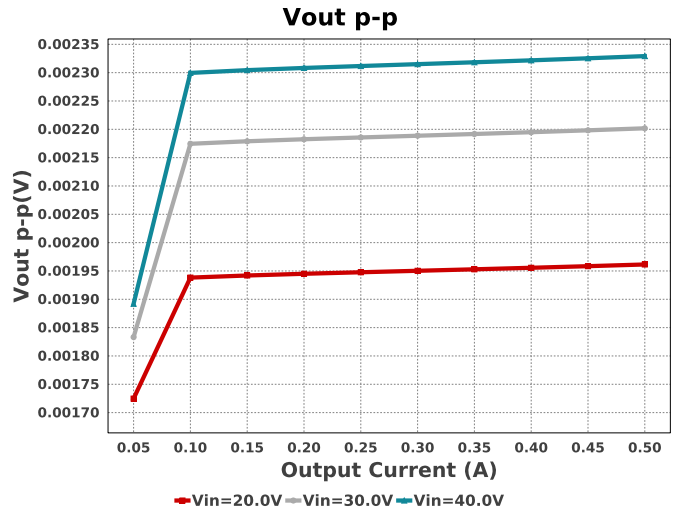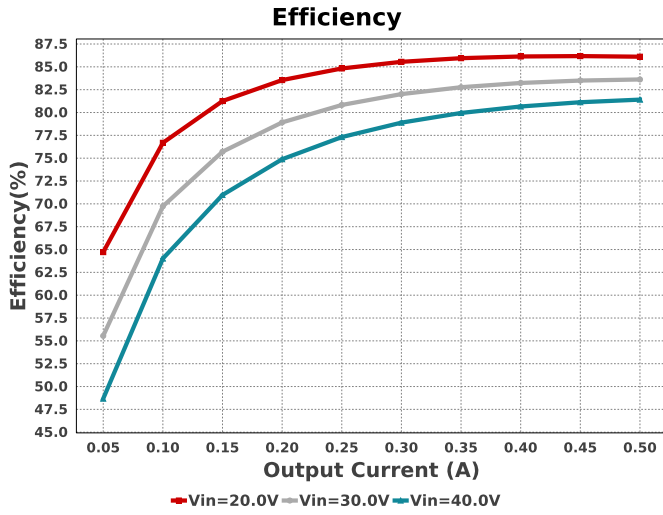

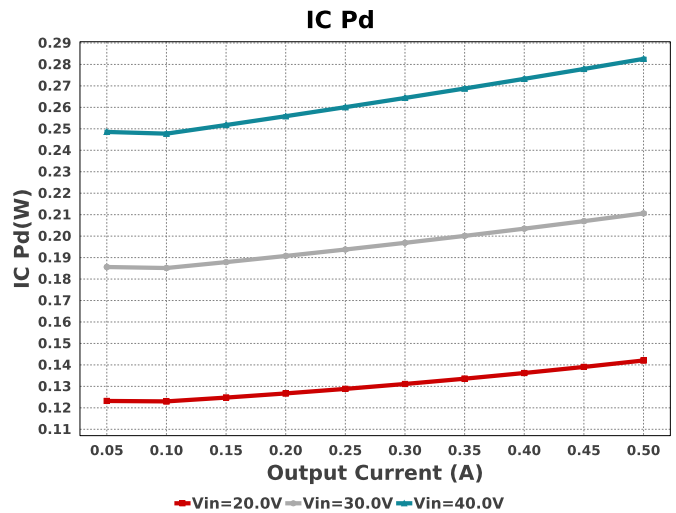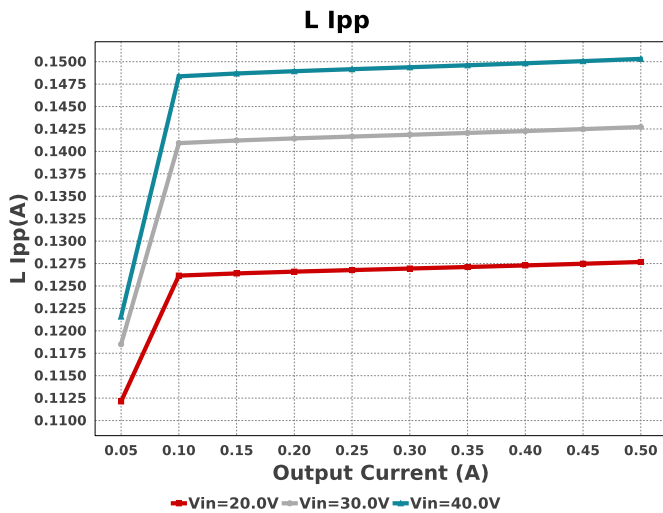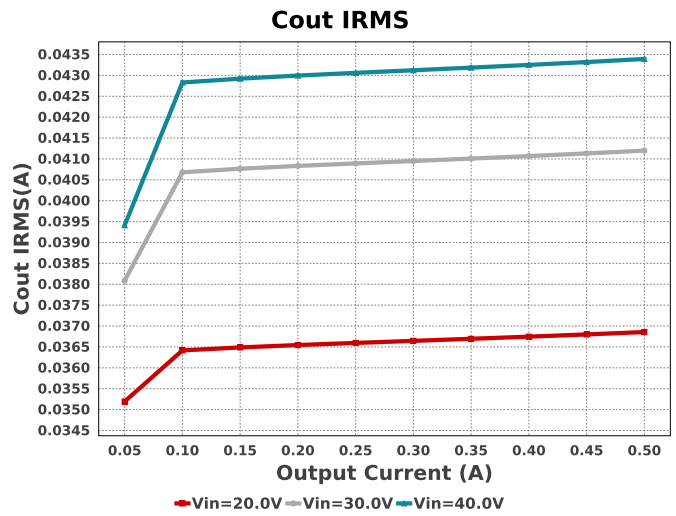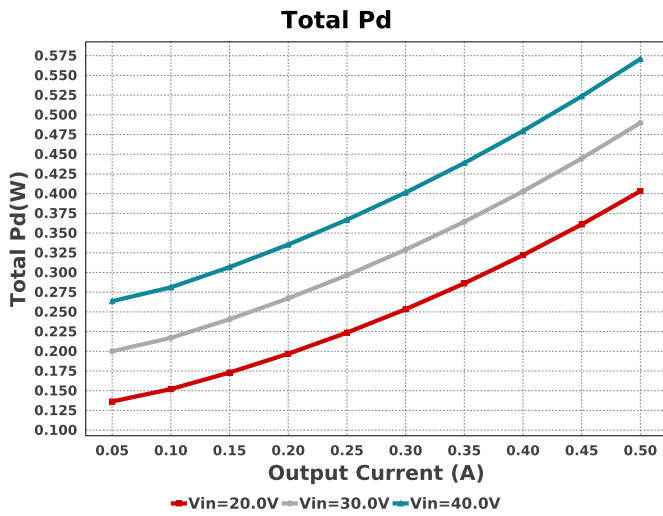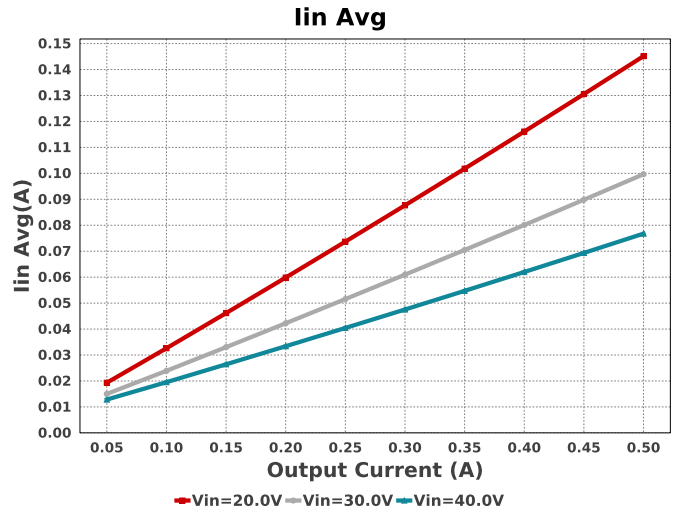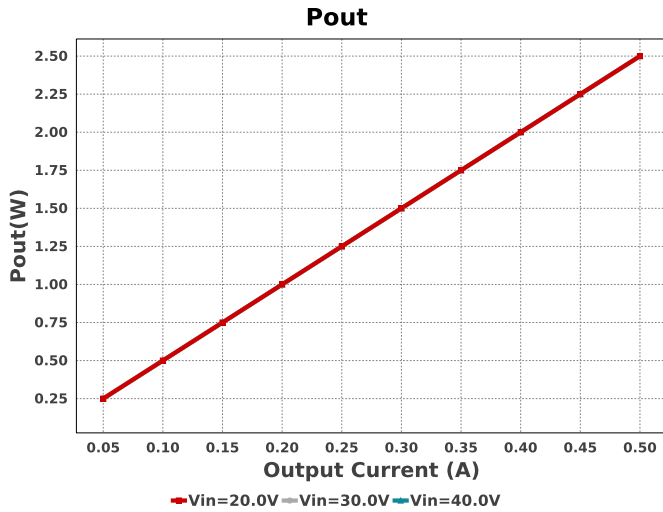

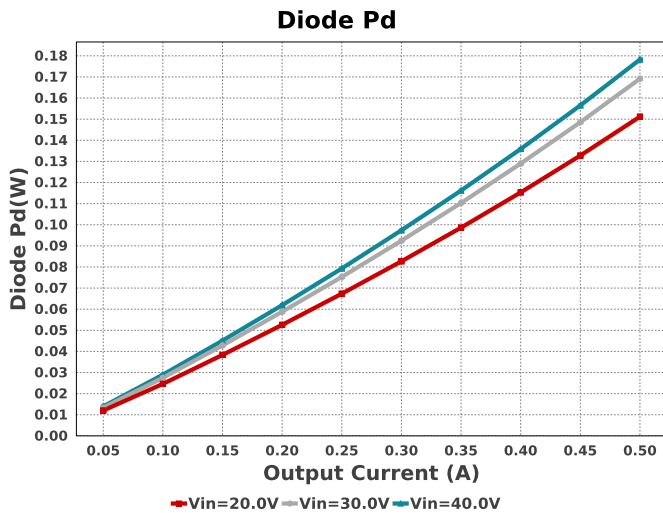

## Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	156.865 mA	Capacitor	Input capacitor RMS ripple current
2.	Cin Pd	12.303 $\mu$ W	Capacitor	Input capacitor power dissipation
3.	Cout IRMS	43.392 mA	Capacitor	Output capacitor RMS ripple current
4.	Cout Pd	5.718 $\mu$ W	Capacitor	Output capacitor power dissipation
5.	D1 Tj	88.824 degC	Diode	D1 junction temperature
6.	Diode Pd	178.25 mW	Diode	Diode power dissipation
7.	IC Ipk	0.0 A	IC	Peak switch current in IC
8.	IC Pd	282.59 mW	IC	IC power dissipation
9.	IC Tj	37.347 degC	IC	IC junction temperature
10.	IC Tolerance	100.0 mV	IC	IC Feedback Tolerance
11.	ICThetaJA	26.0 degC/W	IC	IC junction-to-ambient thermal resistance
12.	Iin Avg	76.771 mA	IC	Average input current
13.	L Ipp	150.32 mA	Inductor	Peak-to-peak inductor ripple current
14.	L Pd	110.0 mW	Inductor	Inductor power dissipation
15.	M Irms	183.027 mA	Mosfet	MOSFET RMS ripple current
16.	M Vds Act	24.675 mV	Mosfet	Voltage drop across the MosFET
17.	Cin Pd	12.303 $\mu$ W	Power	Input capacitor power dissipation
18.	Cout Pd	5.718 $\mu$ W	Power	Output capacitor power dissipation
19.	Diode Pd	178.25 mW	Power	Diode power dissipation
20.	IC Pd	282.59 mW	Power	IC power dissipation
21.	L Pd	110.0 mW	Power	Inductor power dissipation
22.	Total Pd	570.838 mW	Power	Total Power Dissipation
23.	BOM Count	8	System	Total Design BOM count
				Information
24.	Cross Freq	23.265 kHz	System	Bode plot crossover frequency
				Information
25.	Duty Cycle	13.4 %	System	Duty cycle
				Information
26.	Efficiency	81.411 %	System	Steady state efficiency
				Information
27.	FootPrint	409.0 mm <sup>2</sup>	System	Total Foot Print Area of BOM components
				Information
28.	Frequency	260.0 kHz	System	Switching frequency
				Information
29.	Iout	500.0 mA	System	Iout operating point
				Information
30.	Mode	CCM	System	Conduction Mode
				Information
31.	Phase Marg	42.43 deg	System	Bode Plot Phase Margin
				Information
32.	Pout	2.5 W	System	Total output power
				Information
33.	Total BOM	\$4.09	System	Total BOM Cost
				Information
34.	Vin	40.0 V	System	Vin operating point
				Information
35.	Vout	5.0 V	System	Operational Output Voltage
				Information
36.	Vout Tolerance	2.0 %	System	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
				Information
37.	Vout p-p	2.329 mV	System	Peak-to-peak output ripple voltage
				Information

## Design Inputs

Name	Value	Description
Iout	500.0 m	Maximum Output Current
VinMax	40.0	Maximum input voltage
VinMin	20.0	Minimum input voltage
Vout	5.0	Output Voltage
base_pn	LM2678	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature

## WEBENCH® Assembly

### Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of  $C_{in}$  and  $C_{out}$ , and the inductance and DC resistance of  $L1$  before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

### Soldering Component to Board

If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

### Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 20.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to  $V_{in}$  and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from  $V_{out}$  and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

### Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between  $V_{in}$  and GND, a load is connected between  $V_{out}$  and GND and a current meter is connected in series between  $V_{out}$  and the load. The load must be able to handle at least rated output power + 50% ( 7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.

